

Question 1 (30 minutes – 3 points) 2016-17 Midterm exam (ICs)

- Draw the transistor level CMOS circuit for the following logic function, using the lowest possible number of transistors: $S = (A + \overline{B})\overline{C}$
- Draw a 2-input multiplexer using transmission gates at the transistor level. Use the multiplexer, as many times as necessary, to implement the logic function: $S = A\overline{B}$

Question 2 (20 minutes – 2 points) 2016-17 Midterm exam (ICs)

- Explain briefly the thermal oxidation and photolithography processes in relation with integrated circuits manufacturing.
- Explain the utility of design rules and give two examples.

Question 1 (40 minutes – 3 points) 2015-16 Midterm exam (ICs)

For the circuit of the figure:

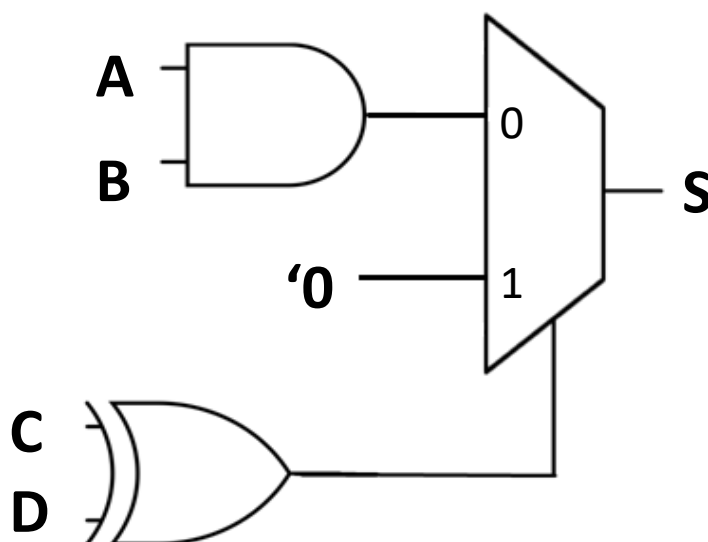


Figure Q1

- Implement the corresponding schematic at transistor level with transmission gates and inverters.
- Which is the main advantage of using transmission gates instead of pass transistors?

Question 2 (20 minutes – 2 points) 2015-16 Midterm exam (ICs)

- Explain the main differences between CMOS and NMOS technology in terms of power consumption and delay.
- Why are the design rules necessary? What is the meaning of the characteristic λ parameter?

Exercise 2 (30 min, 3 points) 2018-19 Midterm exam (ICs)

- Draw the transistor level CMOS circuit for the following logic function, using the lowest possible number of transistors: $S = (\overline{A} \cdot C) + \overline{B}$
- Implement the previous function using transmission gates and inverter.
- Which are the advantages of CMOS technology over NMOS technology?

Question

Given the following CMOS circuit:

- Get your logical expression.
- Create the truth table for the above circuit indicating for each combination the mode of operation of each transistor.

