 



Enhancement NMOS



$$K = \frac{1}{2} \mu_n C_{ox} \frac{W}{L}$$


W=> Width
L=> Length
C_{ox}=> Oxide Capacitance
μ_n=> Electron Mobility

*V_t = Threshold voltage

 

- Cut-off : $v_{GS} < *V_t$
 $i_{DS} = 0$
- Triode: $v_{DS} < v_{GS} - v_t$
 $i_{DS} = K[2(v_{GS} - v_t) v_{DS} - v_{DS}^2]$
- Saturation: $v_{DS} > v_{GS} - v_t$
 $i_{DS} = K (v_{GS} - v_t)^2$

Depletion NMOS

 


- Pre-manufactured channel

$v_{GS} = 0$ Conduction

$v_{GS} < -v_t$ Channel disappears

NMOS Loads

- Enhancement load:

 


$$v_{DG} = 0$$

$$v_{DS} = v_{GS}$$

- Cut-off : $v_{GS} < v_t$
- Otherwise, Saturation always


Device acts as a Nonlinear resistor !!!

- Depletion load:

 


$$v_{GS} = 0$$

Conduction always
(Triode or Saturation)


 


NMOS Inverter


Resistive Load

 

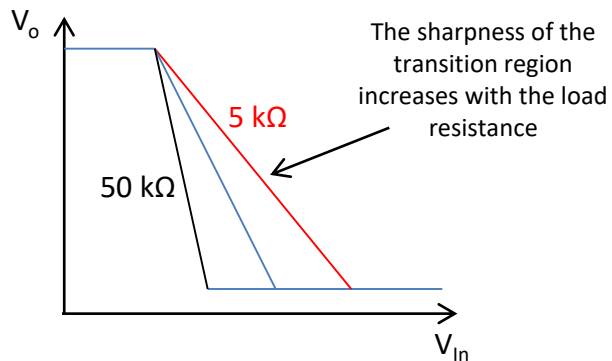 
$$v_{In} = 0V \rightarrow v_{In} < v_t \quad v_{In} = V_{DD}$$




Enhancement Load

 

 
- Much more practical than the resistor loaded inverter, because the resistors are thousand of times larger size than a MOSFET.
- Wide range of inputs where the output is not determined




Depletion Load

 

 - The dynamic margin is much better even though the W/L ratio for the output is small.



NMOS Logic Gates

 


NMOS logic circuits are constructed by connecting driver transistors in **parallel**, **series** or **combinations** to produce required output logic function.

- Transistors in **serial** make **logic products**
- Transistors in **parallel** make **logic additions**
- Output is **inverted**
 - 2 transistors in **serial** make a **NAND** gate
 - 2 transistors in **parallel** make a **NOR** gate

NMOS Logic Gates

 
$$\text{NAND GATE } f = \overline{a \cdot b}$$




a	b	f
0	0	1
0	1	1
1	0	1
1	1	0



a=0 b=1

 

a=1 b=1

 


- Transistors in **serial** make **logic products**
- Transistors in **parallel** make **logic additions**
- Output is **inverted**


NMOS Logic Gates

NOR GATE $f = \overline{a+b}$


a	b	f
0	0	1
0	1	0
1	0	0
1	1	0

 

$f = \overline{(a \cdot b) + c}$

 


$f = \overline{(a+b) \cdot c}$

 


- Transistors in **serial** make **logic products**
- Transistors in **parallel** make **logic additions**
- Output is **inverted**

NMOS gates characteristics


Propagation delay

 

 
Transitions are not perfect, they are delayed because of **parasitic capacitances** and **resistors**. The considered model for the NMOS inverter is:




Calculation of τ_{PHL}

 

 
$$\tau_{PHL} = (R_L \parallel R_{ON}) \cdot C_L$$



Calculation of τ_{PLH}

 

$$\tau_{PLH} = R_L C_L$$

 


$$\tau_{PLH} \gg \tau_{PHL}$$

Asymmetric propagation times


NMOS gates characteristics

Power Consumption

 There is static power consumption in NMOS technologies



No consumption!!!!
(high output)

 

Consumption!!!!
(low output)

A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0



25% of cases drain power

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

75% of cases drain power



- Better implementation of NMOS circuits with NAND than NOR
- NMOS technologies are not commonly used because of the static power consumption

PMOS

  


- Same equations than NMOS, changing current and voltage signs
- Not widely used as NMOS because hole mobility (PMOS) is lower than electron mobility (NMOS)
- To get the same current, usually we need a bigger transistor ($\mu_n = 2.5 \cdot \mu_p$)

Complementary MOS Technologies (CMOS)

  


- CMOS has replaced NMOS at all level of integration because power dissipation in CMOS logic circuits is much lower than in NMOS circuits.
- Instead of using a load, we use a dual network with NMOS and PMOS.


CMOS Inverter

 

$V_{in} = '0'$

 


$V_{in} = '1'$

 

CMOS logic Gates


NAND GATE $f = \overline{a \cdot b}$

 


a	b	f
0	0	1
0	1	1
1	0	1
1	1	0



$a=0 \ b=1$

 


$a=1 \ b=1$

 


CMOS Logic Gates


NOR GATE $f = \overline{a+b}$

 

$f = \overline{(a \cdot b) + c}$

 

$f = \overline{D + A \cdot (B + C)}$

 


Looking at NMOS:


- Transistors in **serial** make **logic products**
- Transistors in **parallel** make **logic additions**
- Output is **inverted**

CMOS gates characteristics

Delay

 

(a) Low-to-high

 

(b) High-to-low

$$t_{pHL} = f(R_{on} \cdot C_L) \\ = 0.69 R_{on} C_L$$


We can manufacture
transistors so that $R_p = R_n$

$$\tau_{PLH} = \tau_{PHL}$$

Symmetric propagation times

CMOS gates characteristics

Power Consumption

 

➤ A=> NMOS Cut-off

No power

➤ B=> NMOS Ohmic
PMOS Sat

Consumption
limited by N

➤ C=> NMOS Sat
PMOS Sat

High
Consumption

➤ D=> NMOS Sat
PMOS Ohmic

Consumption
limited by P

➤ E=> PMOS Cut-off

No power

$$P_{\text{dynamic}} = \text{freq} \cdot C \cdot V_{DD}^2$$

CMOS gates characteristics



Logic gates Size

- We know that $\mu_n = 2.5 \cdot \mu_p$
- Usually transistors are designed so that L is as small as possible
 - $L_n = L_p$
 - W must be different => Width of P must be bigger
 - $\frac{1}{2} \frac{W_n}{L_n} \mu_n C_{ox} = \frac{1}{2} \frac{W_p}{L_p} \mu_p C_{ox}$
- PMOS transistors need to be 2.5 times (W) bigger than NMOS

Pass transistors

Use of transistors as switches between driving circuits and load circuits are called **pass transistors**

NMOS

  


$$V_{DS} = V_{DG} - V_{GS} = 0 + V_{GS}$$

$$V_{GS} > V_t \rightarrow V_{DS} > V_t$$

$$V_D - V_S > V_t \rightarrow V_S < V_D - V_t$$

$$V_S = 1 - V_t \quad \text{Degradation!!!}$$

PMOS

 


C	A	f
0	0	V_t
0	1	1
1	0	Z
1	1	Z

"weak" '0'

CMOS Transmissions gates

- A CMOS transmission gate can be constructed by parallel combination of NMOS and PMOS with complementary gate signals.
- The main advantage of the CMOS transmission gate compared to pass transistors is to allow the input signal to be transmitted to the output without the threshold voltage attenuation

 
4 Transistors => 2 transmission gate; 2 Inverter



C	A	f
0	0	Z
0	1	Z
1	0	0
1	1	1

} A


Triestate buffer

 

CMOS Transmissions gates

C=0	A=0	$V_{GSn} = 0 - 0 \longrightarrow$ Cut-off
		$V_{GSp} = 5 - 0 \longrightarrow$ Cut-off
	A=1	$V_{GSn} = 0 - 5 \longrightarrow$ Cut-off
		$V_{GSp} = 5 - 5 \longrightarrow$ Cut-off


C=1	A=0	$V_{GSn} = 5 - 0 \longrightarrow$ Conduction
		$V_{GSp} = 0 - 0 \longrightarrow$ Cut-off
	A=1	$V_{GSn} = 5 - 5 \longrightarrow$ Cut-off
		$V_{GSp} = 0 - 5 \longrightarrow$ Conduction

 

- $C='0'$, \Rightarrow High impedance, both transistors are cut-off
- $C='1'$, $A='0'$ \Rightarrow N conducts \Rightarrow Puts '0'
- $C='1'$, $A='1'$ \Rightarrow P conducts \Rightarrow Puts '1'


Logic gates with Transmissions gates

Multiplexer

 


C	A	B	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

} A
} B

 

$C=0 \rightarrow f=A$


$C=1 \rightarrow f=B$

 

6 transistors
 4 for Transmission gates
 2 for Inverter

Logic gates with Transmissions gates


XOR

 

A	B	f
0	0	0
0	1	1
1	0	1
1	1	0

} B
} \overline{B}




8 Transistors!!!!

 

A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

C	X	S
0	0	0
0	1	1
1	0	1
1	1	1

} B
} 1

   

Logic gates with Transmissions gates

D-latch (level triggered bistable)

