



**Universidad
Carlos III de Madrid**

VHDL: Digital Circuits


MEMORY CIRCUITS

Outline

- ❑ Memory circuits review
- ❑ Memory circuits design
- ❑ Memory circuits synthesis

Memory circuits review

Basic Interface

 

Memory circuits review

- Address bus (A): Sets the position to access
 - ❖ n bits wide for a memory with 2^n positions
 - ❖ Example: 20 bits for 1M, 30 bits for 1G
- Data bus (D): Provides the datum
 - ❖ Data bus width (m) is equal to data size
 - ❖ Input data for writing
 - ❖ Output data for reading
 - ❖ Can be a single bidirectional bus, or two buses, one input bus and one output bus

Memory circuits review

- Control bus: signals that control memory operation. Some typical signals:
 - ❖ CS (Chip Select) or CE (Chip Enable): when deasserted, data bus is typically in tristate mode
 - ❖ R/W (Read/Write) or WE (Write Enable): selects the memory operation (read or write)
 - ❖ OE (Output Enable): Enables data output. When deasserted, data bus is typically in tristate mode
 - ❖ RAS (Row Address Strobe) and CAS (Column Address Strobe) in memories with 3D organization
 - ❖ Other signals: CLK in synchronous memories, BE (Byte Enable) to select particular bytes in a memory word, etc.

Memory circuits review

Semiconductor memory circuits

❑ RAM memory (Random Access Memory)

- ❖ Memories for reading and writing
- ❖ Example: computer main memory

❑ ROM memory (Read Only Memory)

- ❖ Read only memory
- ❖ Contents fixed during manufacturing or programmable
- ❖ Example: Flash memory

Memory circuits review

RAM Memory

- Read & Write memory

- Two main types:

- ❖ Static RAM (SRAM): every bit is stored in a bistable
- ❖ Dynamic RAM (DRAM): every bit is stored in a capacitor

- Currently, the most widely used type of DRAM is DDR (Double Data Rate) SDRAM

- ❖ 3D organization
- ❖ Clocked memory (Synchronous DRAM)
- ❖ Data access in both clock edges (Double Data Rate)
- ❖ 64 bits wide data
- ❖ Versions evolving on time: DDR, DDR2, DDR3, DDR4

Memory circuits review

ROM Memory


- ❑ Read Only Memory
- ❑ Non volatile
- ❑ Types
 - ❖ Mask programmable: contents fixed by manufacturing
 - ❖ One-Time Programmable: contents fixed by the user
 - ❖ Erasable or Reprogrammable: can be erased to store new contents
- ❑ The concepts of “writing” and “programming” should be distinguished, although the frontier is becoming blurred:
 - ❖ Writing is an operation similar to reading
 - ❖ Programming uses physical means different from reading, it is generally slower and it must be applied on a block basis or even for the entire chip

Memory circuits review

- ❑ Synchronous/asynchronous
- ❑ Single Port: Only one access (read/write) per clock cycle.
- ❑ Double Port: Two address and control buses. Two addresses can be accessed simultaneously.
- ❑ LIFO (Last Input First Output) and FIFO (First Input First Output). They may be single or double port.


Last Input First Output Memory (LIFO)

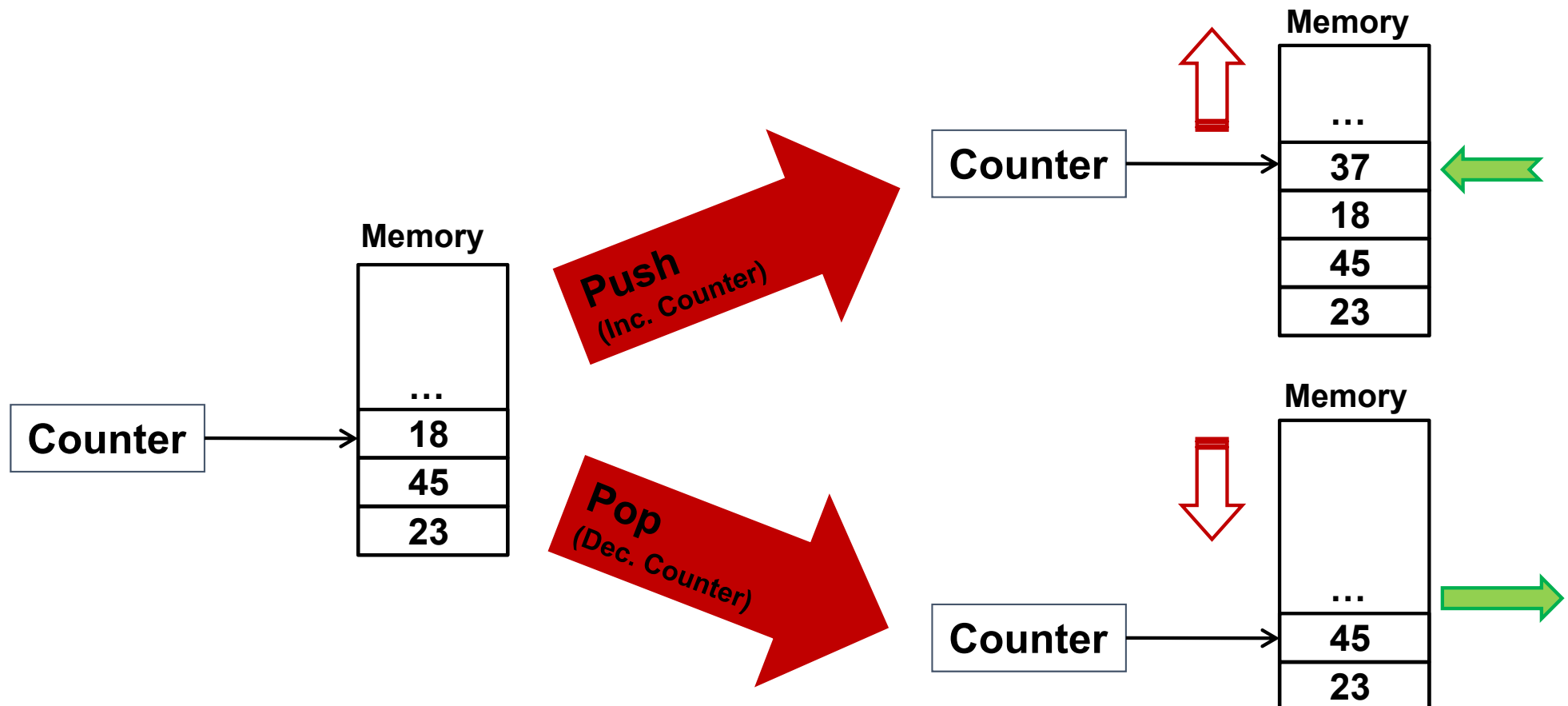- LIFO (Last In First Out): Implements a stack.




First Input First Output Memory (FIFO)

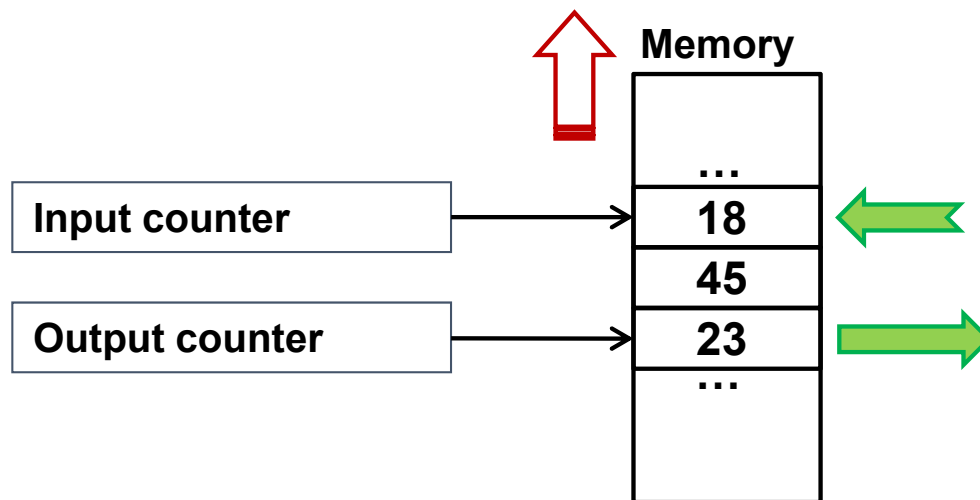- ❑ FIFO (First In First Out): Data get in and out in the same sort order, but at different instants
- ❑ Application: Temporary storage for reading a data burst



FIFO/LIFO example: Interface

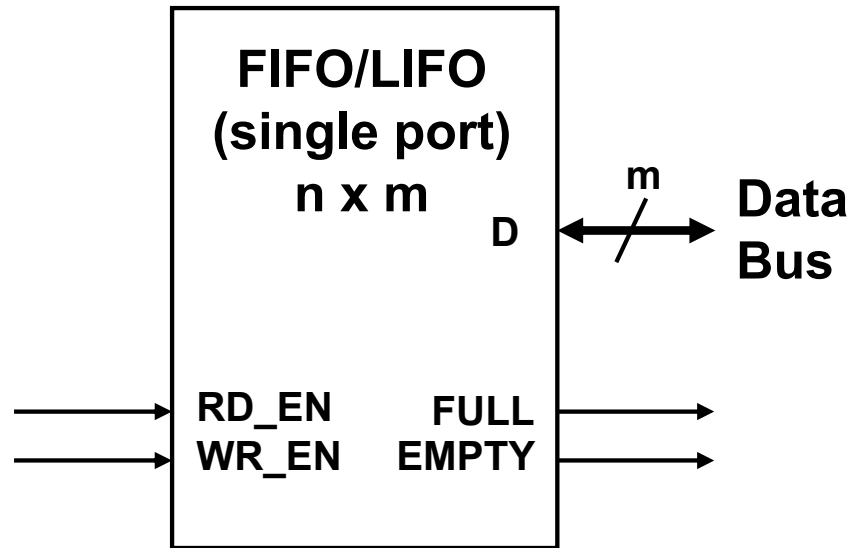

- ❑ n: size, maximum number of data that can be written in the FIFO/LIFO
- ❑ RD_EN/WR_EN: Used to activate a read/write.
- ❑ FULL/EMPTY: Indicate whether the memory is empty (no more data can be read) or full (no more data can be written)

Memory circuits synthesis

❑ Distributed memory

❖ Using flip-flops

- Independent of the technology.
- Synchronous writing, asynchronous reading
- They may have high area requirements

❖ Using LUTs (Look-up tables)

- Dependent of the techonolgy (they need to be available in the target device).
- Synchronous writing, asynchronous reading

❑ Dedicated memory blocks

❖ Dependent of the techonology

❖ Synchronous reading and writing

❑ Each manufacturer provides the necessary means:

- Synthesis tools
- Synthesis directives
- Libraries and code generators (example: Xilinx Core Generator)

Example: Asynchronous ROM

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity rom_example is
    port (address : in  integer range 0 to 255;
          data_o   : out std_logic_vector(7 downto 0))
    );
end rom_example;

architecture behavioral of rom_example is

    type rom_t is array (0 to 255) of std_logic_vector(7 downto 0);
    signal rom : rom_t := (
        X"FF", -- address = 0
        X"01", -- address = 1
        X"34", -- address = 2
        X"87",
        . . .
    );

begin

    data_o <= rom(address);

end behavioral;
```

❑ It can be implemented only as distributed memory

Example: RAM with asynchronous reading

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ram_example is
    port (Clk      : in  std_logic;
          address  : in  integer range 0 to 255;
          we       : in  std_logic;
          data_i   : in  std_logic_vector(7 downto 0);
          data_o   : out std_logic_vector(7 downto 0)
    );
end ram_example;

architecture behavioral of ram_example is

    type ram_t is array (0 to 255) of std_logic_vector(7 downto 0);
    signal ram : ram_t := (others => (others => '0'));

begin

    data_o <= ram(address);

    process(Clk)
    begin
        if rising_edge(Clk) then
            if (we='1') then
                ram(address) <= data_i;
            end if;
        end if;
    end process;

end behavioral;
```

□ Asynchronous reading, synchronous writing: it can be only distributed memory

Example: RAM with synchronous reading

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ram_example is
    port (Clk      : in  std_logic;
          address  : in  integer range 0 to 255;
          we       : in  std_logic;
          data_i   : in  std_logic_vector(7 downto 0);
          data_o   : out std_logic_vector(7 downto 0)
    );
end ram_example;

architecture behavioral of ram_example is

    type ram_t is array (0 to 255) of std_logic_vector(7 downto 0);
    signal ram : ram_t := (others => (others => '0'));

begin

    process(Clk)
    begin
        if rising_edge(Clk) then
            if (we='1') then
                ram(address) <= data_i;
            end if;
            data_o <= ram(address);
        end if;
    end process;

end behavioral;
```

- ❑ Synchronous reading and writing: it can be distributed or block
- ❑ “Read first”: reading returns the previous value to the one that is being written